

Gate Questions on Multiplexers (MUX)


October 20, 2017 2 comments

Gate Questions on Multiplexers (MUX)

1992

Question 1: GATE | GATE-EC-1992

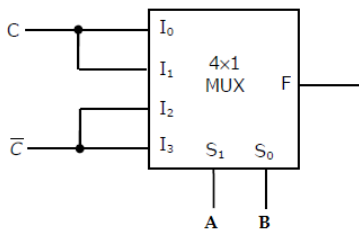The logic realized by the circuit shown in figure is -



- (A) $F = A \odot C$
 (B) $F = A \otimes C$
 (C) $F = B \odot C$
 (D) $F = B \otimes C$


Answer: (B)

Explanation:

2001

Question 1: GATE | GATE-EC-2001

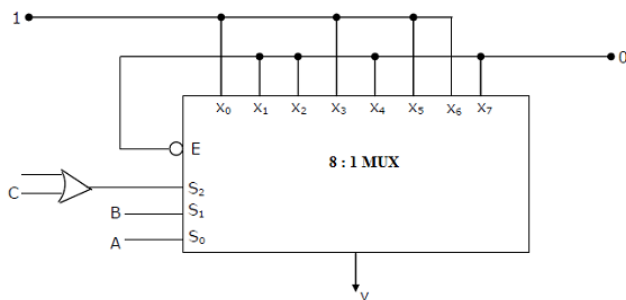In the TTL circuit in the figure, S_2 to S_0 are select lines and X_7 and X_0 are input lines. S_0 and X_0 are LSBs. The output Y is -



- (A) indeterminate
 (B) $A \otimes B$
 (C) $A \otimes B$
 (D) $\bar{C} \cdot (A \otimes B) + C \cdot (A \otimes B)$

Answer: (D)

Explanation:

2003

Question 1: GATE | GATE-EC-2003 (ISRO-EC-2017)

Without any additional circuitry, an 8:1 MUX can be used to obtain -

- (A) some but not all Boolean functions of 3 variables
 (B) all function of 3 variables but none of 4 variables
 (C) all functions of 3 variables and some but not all of 4 variables
 (D) all functions of 4 variables

Answer: (C)

Explanation:

2004

Question 1: GATE | GATE-EC-2004

The minimum number of 2 to 1 multiplexers required to realize a 4 to 1 multiplexer is -

- (A) 1
 (B) 2

SOCIAL PROFILES



Search

Popular

Tags

Blog Archives

GATE ASPIRANTS

Dear GATE Aspirants, This Blog is for the students who want to do self study for GATE, ISRO, DRDO, BARC, PSUs and other competitive examination. Please go to the subject chapter-wise as per given in the drop-down list. Read it carefully and **note down all the important concepts and Formulae in your note-book.** Practice more and more on questions, therefore at the end of each chapter of every subject, Objective type questions are given. GATE questions also given at the end of the chapter.

GATE 2019 QUESTIONS-ANSWERS

General Aptitude

Engineering Mathematics

Electronic Devices

Analog Circuits

Digital Electronics

Microprocessor(8085)

Network Systems

Signals and Systems

Control Systems

Communication Systems

Electromagnetic Theory

POPULAR POSTS

Topicwise Previous Year GATE Questions on Microprocessor 8085

Microprocessor(8085) Topicwise Previous Year GATE Questions(1987-2017) Gate Questions on Fundamentals of Microprocessor Ga...

Gate Questions on Fundamentals of Microprocessor

Gate Questions on Fundamentals of Microprocessor 1995 Question 1: GATE | GATE-EC-1995 An 'Assembler' of a microp...

Gate Questions on Instruction Set of 8085

Gate Questions on Instruction Set of 8085 1988 Question 1: GATE | GATE-EC-1988 In register index addressing mode...

- (C) 3
(D) 4

Answer: (C)

Explanation:

Question 2: GATE | GATE-CS-2004

Consider a multiplexer with X and Y as data inputs and Z as control input. Z = 0 selects input X, and Z = 1 selects input Y. What are the connections required to realize the 2-variable Boolean function $f = T + R$, without using any additional hardware ?

- (A) R to X, 1 to Y, T to Z
(B) T to X, R to Y, T to Z
(C) T to X, R to Y, 0 to Z
(D) R to X, 0 to Y, T to Z


Answer: (A)

Explanation:

2005

Question 1: GATE | GATE-EC-2005

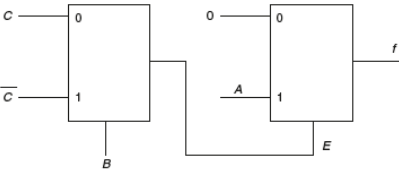The Boolean function f implemented in figure using two input multiplexers is -



- (A) $\bar{A}\bar{B}C + AB\bar{C}$
(B) $ABC + \bar{A}\bar{B}\bar{C}$
(C) $\bar{A}BC + \bar{A}\bar{B}\bar{C}$
(D) $\bar{A}BC + \bar{A}B\bar{C}$


Answer: (A)

Explanation:

2007

Question 1: GATE | GATE-EC-2007

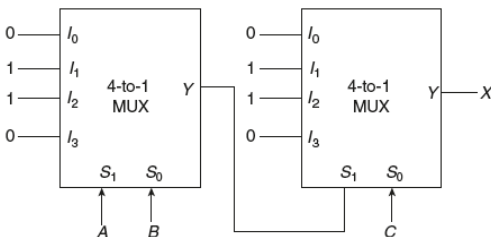In the following circuit, X is given by -



- (A) $X = A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$
(B) $X = \bar{A}BC + A\bar{B}C + AB\bar{C} + \bar{A}\bar{B}\bar{C}$
(C) $X = AB + BC + AC$
(D) $X = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}$


Answer: (A)

Explanation:

2008

Question 1: GATE | GATE-EC-2008

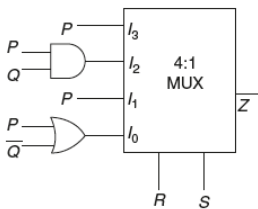For the circuit shown in the following figure I_0 - I_3 are inputs to the 4:1 multiplexer R(MSB) and S are control bits. The output Z can be represented by -



- (A) $PQ + P\bar{Q}S + \bar{Q}\bar{R}\bar{S}$
(B) $P\bar{Q} + PQR + \bar{P}\bar{Q}\bar{S}$
(C) $P\bar{Q}\bar{R} + \bar{P}QR + PQR\bar{S} + \bar{Q}\bar{R}\bar{S}$
(D) $PQR + PQR\bar{S} + P\bar{Q}\bar{R}S + \bar{Q}\bar{R}\bar{S}$



Gate Questions on Memory and I/O Interfacing of 8085

Gate Questions on Memory and I/O Interfacing of 8085 1988 Question 1: GATE | GATE-EC-1988 A microprocessor with ...

1

GATE Questions on Laplace Transform

Gate Questions on Laplace Transform 1987 Question 1: GATE | GATE-EC-1987 Laplace transform of the functions $t u(t)$ a...

Gate Questions on Architecture of 8085

Gate Questions on Architecture of 8085 1989 Question 1: GATE | GATE-EC-1989 In a microprocessor system, the stack...



Gate Questions on Multiplexers (MUX)

Gate Questions on Multiplexers (MUX) 1992 Question 1: GATE | GATE-EC-1992 The logic realized by the circuit sho...

Gate Questions on Pins and Signals of 8085

Gate Questions on Pins and Signals of 8085 1993 Question 1: GATE | GATE-EC-1993 In a microcomputer, wait states ...



Gate Questions on Flip-flop, Counters and Shift-Registers

1988 Question 1: GATE | GATE-EC-1988 The circuit given below is a - (A) J-K Flip-Flop (B) Johnson's Co...

Gate Questions on Number System Representation

1987 Question 1: GATE | GATE-EC-1987 The subtraction of a binary number Y from another binary number X, done by ad...

BLOG ARCHIVE

- ▶ 2019 (16)
- ▶ 2018 (25)
- ▼ 2017 (69)
 - ▶ December (34)
 - ▶ November (17)
 - ▼ October (18)
 - Network Systems
 - Latches and Flip-Flops
 - Digital Electronics
 - Gate Questions on Logic Families
 - Gate Questions on ADC and DAC Converters
 - Boolean Algebra
 - Gate Questions on Combinational Arithmetic Circuit...
 - Logic Gates
 - Gate Questions on Logic Gates
 - Topicwise Previous Year GATE Questions(1987-2019)
 - Gate Questions on Boolean Algebra
 - Gate Questions on Multiplexers (MUX)
 - Number System
 - Gate Questions on Floating Point Representation
 - Combinational Circuits
 - Gate Questions on Number System Representation
 - Sequential Circuits
 - Gate Questions on Flip-flop, Counters and Shift-Re...

Answer: (A)
Explanation:

2009

Question 1: GATE | GATE-EC-2009

What are the minimum number of 2 to 1 multiplexers required to generate a 2-input AND gate and a 2-input Ex-OR gate?

- (A) 1 and 2
- (B) 1 and 3
- (C) 1 and 1
- (D) 2 and 2


Answer: (A)

Explanation:

2010

Question 1: GATE | GATE-EC-2010

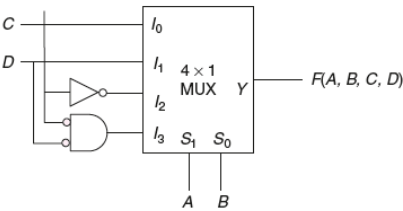The Boolean function realized by the logic circuit shown is -



- (A) $F = \sum m(0,1,3,5,9,10,14)$
- (B) $F = \sum m(2,3,5,7,8,12,13)$
- (C) $F = \sum m(1,2,4,5,11,14,15)$
- (D) $F = \sum m(2,3,5,7,8,9,12)$


Answer: (D)

Explanation:

2011

Question 1: GATE | GATE-EC-2011

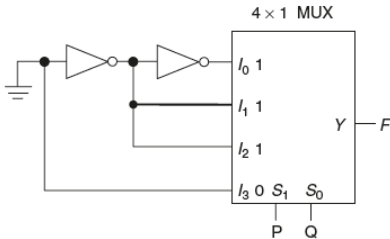The logic function implemented by the circuit below is (ground implies logic 0)-



- (A) $F = \text{AND}(P,Q)$
- (B) $F = \text{OR}(P,Q)$
- (C) $F = \text{XNOR}(P,Q)$
- (D) $F = \text{XOR}(P,Q)$


Answer: (D)

Explanation:

2014

Question 1: GATE | GATE-EC-2014

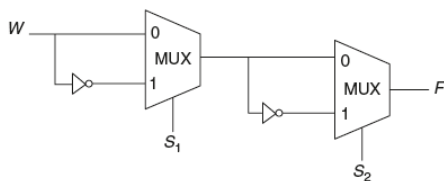Consider the multiplexer-based logic circuit shown in the figure.




Which one of the following Boolean functions is realized by the circuit?

- (A) $F = W \overline{S_1} \overline{S_2}$
- (B) $F = WS_1 + WS_2 + S_1S_2$
- (C) $F = W + S_1 + S_2$

► 2013 (4)

FOLLOWERS

Followers (27) [Next](#)

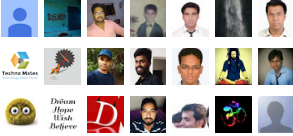

[Follow](#)

ABOUT ME



[SAMS](#)

Hi Friends, Sams here to share you a joy of the success in life...

[VIEW MY COMPLETE PROFILE](#)

Powered by Blogger.

SEARCH THIS BLOG

Theory Format

The photonic nature of light

Direct and Indirect Band Gap

Energy of an Electron

Bohr's Atomic Model

Theory Format

The photonic nature of light

Direct and Indirect Band Gap

Energy of an Electron

Bohr's Atomic Model

FEATURED POSTS

Report Abuse

► Details

► Details

BLOGGER TEMPLATES


(D) $F = W \oplus S_1 \oplus S_2$

Answer: (D)

Explanation:

Question 2: GATE | GATE-EC-2014

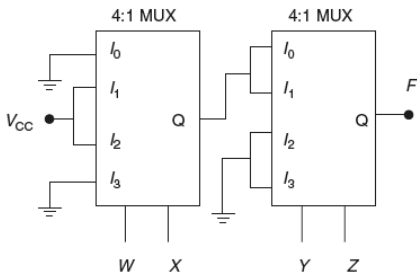In the circuit shown, W and Y are MSBs of the control inputs. The output F is given by -




- (A) $F = W \bar{X} + \bar{W} X + \bar{Y} \bar{Z}$
(B) $F = W \bar{X} + \bar{W} X + \bar{Y} Z$
(C) $F = W \bar{X} \bar{Y} + \bar{W} X \bar{Y}$
(D) $F = (\bar{W} + X) \bar{Y} \bar{Z}$

Answer: (C)

Explanation:

Question 3: GATE | GATE-EC-2014

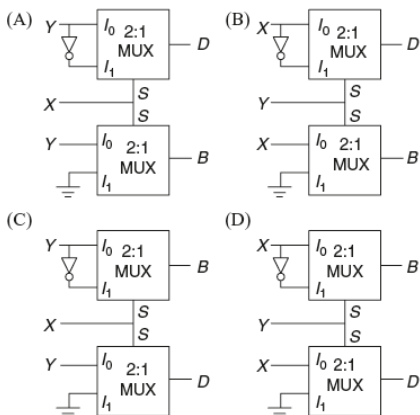If X and Y are inputs and the difference ($D = X - Y$) and the borrow (B) are the outputs, which one of the following diagrams implements a half subtractor?




Answer: (A)

Explanation:

Question 4: GATE | GATE-EC-2014

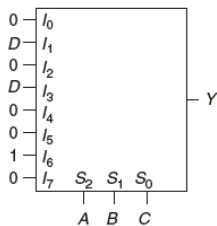An 8-to-1 multiplexer is used to implement a logical function Y, as shown in the figure. The output Y is given by -



- (A) $Y = \bar{A} \bar{B} C + A \bar{C} \bar{D}$
(B) $Y = \bar{A} B \bar{C} + A \bar{B} \bar{D}$
(C) $Y = \bar{A} \bar{B} \bar{C} + \bar{A} \bar{C} \bar{D}$
(D) $Y = \bar{A} \bar{B} \bar{D} + A \bar{B} \bar{C}$

BLOGGER NEWS

ABOUT

ABOUT ME



SAMS

Hi Friends, Sams here to share you a joy of the success in life...

[VIEW MY COMPLETE PROFILE](#)

SUBSCRIBE TO

[Posts](#)

[Comments](#)

PAGES

[Home](#)

ONLINE USERS


Answer: (C)

Explanation:

2015

Question 1: GATE | GATE-EC-2015

A 1-to-8 demultiplexer with data input D_{in} , address inputs S_0, S_1, S_2 (with S_0 as the LSB) and $\overline{Y_0}$ to $\overline{Y_7}$ as the eight demultiplexed outputs, is to be designed using two 2-to-4 decoders (with enable input \overline{E} and address inputs A_0 and A_1) as shown in the figure. D_{in}, S_0, S_1 and S_2 are to be connected to P, Q, R, and S, but not necessarily in this order. The respective input connections to P, Q, R, and S terminals should be -

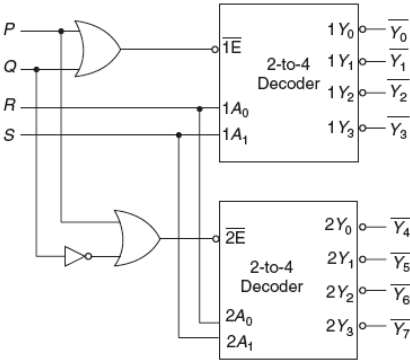

- (A) S_2, D_{in}, S_0, S_1
- (B) S_1, D_{in}, S_0, S_2
- (C) D_{in}, S_0, S_1, S_2
- (D) D_{in}, S_2, S_0, S_1


Answer: (D)

Explanation:

2016

Question 1: GATE | GATE-EC-2016

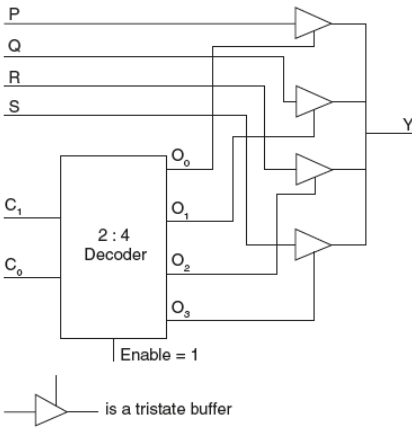The functionality implemented by the circuit below is -




- (A) 2 to 1 multiplexer
- (B) 4 to 1 multiplexer
- (C) 7 to 1 multiplexer
- (D) 6 to 1 multiplexer

Answer: (B)

Explanation:

Question 2: GATE | GATE-EC-2016

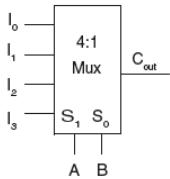A 4:1 multiplexer is to be used for generating the output carry of a full adder. A and B are the bits to be added while C_{in} is the input carry and C_{out} is the output carry. A and B are to be used as the select bits with A being the more significant select bit.



Which one of the following statements correctly describes the choice of signals to be connected to the inputs I_0 , I_1 , I_2 , and I_3 so that the output is C_{out} ?


- (A) $I_0 = 0$, $I_1 = C_{in}$, $I_2 = C_{in}$ and $I_3 = 1$
- (B) $I_0 = 1$, $I_1 = C_{in}$, $I_2 = C_{in}$ and $I_3 = 1$
- (C) $I_0 = C_{in}$, $I_1 = 0$, $I_2 = 1$ and $I_3 = C_{in}$
- (D) $I_0 = 0$, $I_1 = C_{in}$, $I_2 = 1$ and $I_3 = C_{in}$

Answer: (A)

Explanation:

Question 3: GATE | GATE-EC-2016

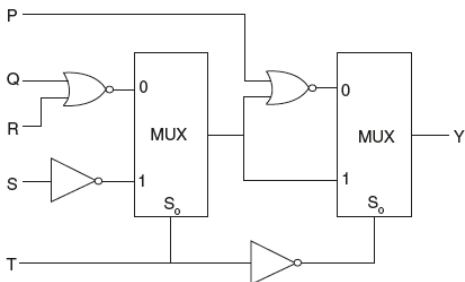For the circuit shown in the figure, the delays of NOR gates, multiplexers and inverters are 2ns, 1.5ns and 1ns respectively. If all the inputs P, Q, R, S and T are applied at the same time instant, the maximum propagation delay (in ns) of the circuit is _____.



Answer: 6 ns

Explanation:



[Newer Post](#)

[Home](#)

[Older Post](#)

2 comments:



[Unknown](#) February 4, 2019 at 9:30 AM

Its very good .Please provide the explanation which helps us to check wheather our analization is true are false

[Reply](#)

▼ [Replies](#)



[Sams](#) February 10, 2019 at 3:53 AM

thank you for appreciating our work. We are working on it to provide the explanation and theory, so that you can easily crack the examination.

[Reply](#)

Enter your comment...



Comment as: Google Account

[Publish](#)

[Preview](#)

